

Experiment 8: Adjustment and Measurement of Power Amplifiers

16231235 李谨杰 Table number: 23

Aim

1. Learn to adjust and measure OTL (output transformerless) power amplifier.
2. Learn to use integrated power amplifiers.

Principle

1. An OTL power amplifier is complementary and symmetrical. In the output there is a capacitor with large capacity instead of a transformer.
2. It has the characteristic of high input resistance and low output resistance, and a low load can be connected to the output directly.
3. Strong negative feedback could be adopted to amend none linear distortion.
4. Bootstrapping circuit is used to improve output amplitude.


Instruments

Digital multimeter, digital oscilloscope, DC power supply, LM386, Power amplifier PCB

Tasks

Tasks -OTL quiescent point adjustment

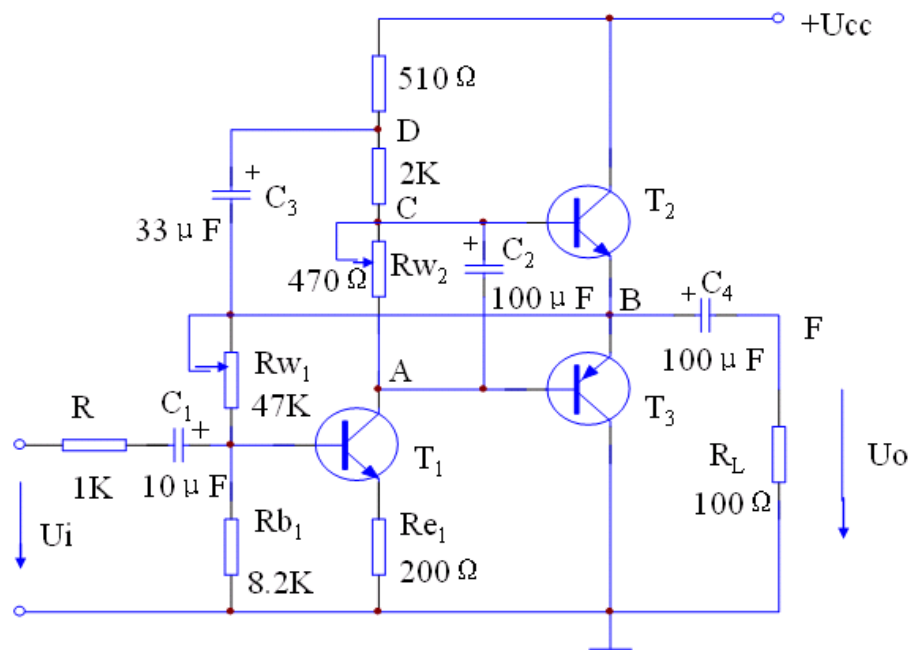1. Turn R_{w1} and R_{w2} anticlockwise to the end first.
2. Get $U_{cc}=12V$.
3. Adjust R_{w1} to make $U_B=6V \sim 6.5V$. (make sure the current value displayed on DC power supply is less than 0.3A. Once it is more than 0.5A, switch off power at once)
4. Put dynamic signal sine wave and $f=1KHz$ to input, and connect input and output to oscilloscope.
5. Increase U_i slowly while adjusting R_{w2} to eliminate cross over distortion.
6. Measure U_A , U_B , U_C , U_D , and calculate $U_{CA}=?$




Circuit1 OTL Circuit

Tasks –OTL AC parameters test

1. Measure P_{omax} and A_v
 - (1) Continue to increase input amplitude gently while watching the output wave. Once distortion waves occur, stop increasing and turn back to the state that the output is just normal.
 - (2) Measure U_i and U_o , and compute P_{omax} and A_v .
2. Measure efficiency
3. The function of C_3 . Watch the waves of output with C_3 and without C_3 . Record and compare.
4. Bootstrapping C_3 improving voltage:
 - (1) Measure voltage of point B, D and U_{CC} .
 - (2) Observe waves of point F, B, D, and U_{CC} , and draw them together on square paper.
5. Observe current waves of T_2 , T_3 on oscilloscope, record and define amplifier's working state.
6. Cross over distortion study: record wave and corresponding quiescent point U_B , U_C , U_A , calculate U_{CA} and compare with previous value.

Tasks--LM386 audio frequency power amplifier circuit

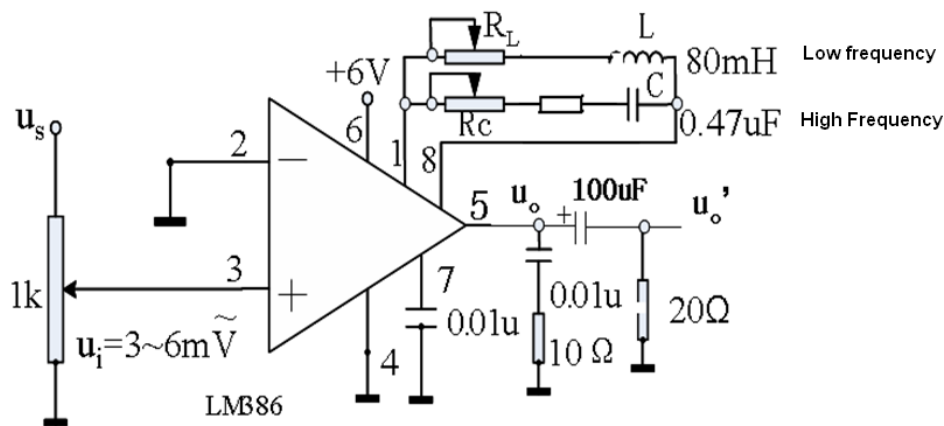1. Build the circuit.
 2. Test the two amplitude frequency characteristics waves
 - (1) $R_L=0\ \Omega$, $R_C=470K\ \Omega$, measure low pass and high attenuating wave at U_o .
 - (2) $R_L=470K\ \Omega$, $R_C=0\ \Omega$ measure low attenuating and high pass wave at U_o .
- Attention: keep $U_i=3\sim6\text{mv}$, $f=20\text{HZ}\sim20\text{KHZ}$, and get 8~10 points.



Circuit2 LM386 audio frequency power amplifier circuit

Data collation and analysis

Task 1

U_A/V	U_B/V	U_C/V	U_D/V	U_{CA}/V
4.753	5.970	7.153	11.067	2.400

Quiescent point is extremely important for power amplifiers. In this experiment, I adjust quiescent point for many times, and I find that the input current would increase sharply if quiescent point is not good.

Task2

U_{CC}/V	I_E/A	U_{ip}/V	U_{op}/V
12.00	0.16	0.27	4.00

$$A_v = \frac{U_o}{U_i} = \frac{4.00}{0.27} = 14.81$$

$$P_{omax} = \frac{U_o^2}{R_L} = \frac{4.00^2}{2 \times 8.1} = 0.988W$$

$$\eta = \frac{p_L}{p_E} = \frac{P_{omax}}{U_{cc} \cdot I_E} = \frac{0.988}{12 \times 0.16} \times 100\% = 51.46\%$$

Task3

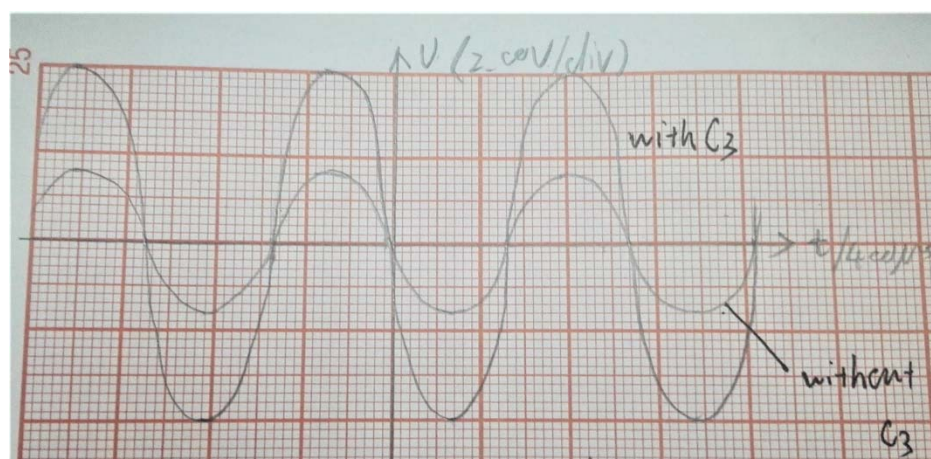


Figure 1 waveform with and without C3

The bigger waveform is with C3. The smaller waveform is without C3. From these waveform, we can conclude that, C3 can enlarge output range.

Task4

U_B/V	U_D/V	U_{VCC}/V
5.978	11.087	12.058

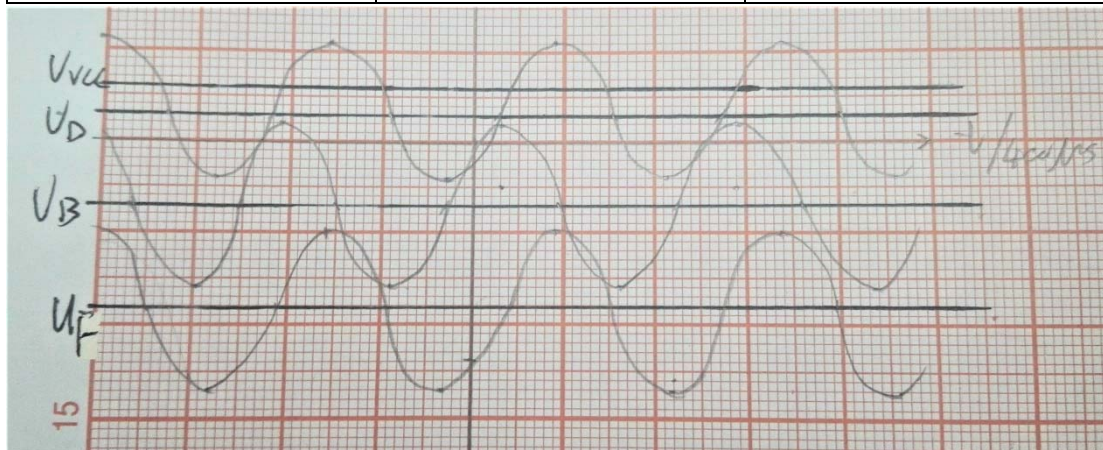


Figure 2 waveform with and without C3

From figure2, the waveform of U_D can be higher than V_{CC} , as the result of capacity C3.

Task 5


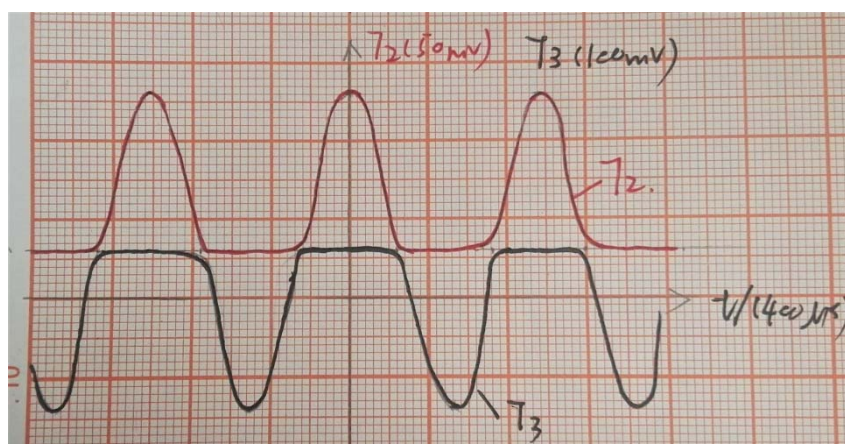


Figure 3 Current waves of T2、T3

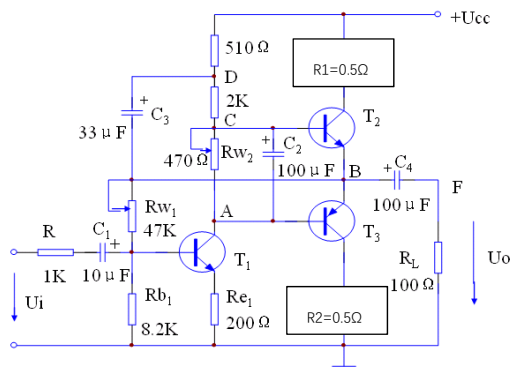The range of T3 is twice of the range of T2. When the waveform is a straight line, triode works in cut-off state; when the waveform is semi-sin-wave, triode works in enlargement state. To explain why the range of two triodes are different is a little difficult. But clever as I still figured it out.



When turn to positive half cycle, U_o is high, so current of R_L is high, then voltage on R_1 is high. As the result, peak voltage is far lower than original peak voltage.

But when turn to negative half cycle, U_o is low, so voltage on R_2 is low. As the result, bottom voltage is a little higher than original bottom peak.

That's the reason why the range is different.

Task 6

U_B/V	U_C/V	U_A/V	U_{CA}/V
6.050	7.063	5.134	1.929

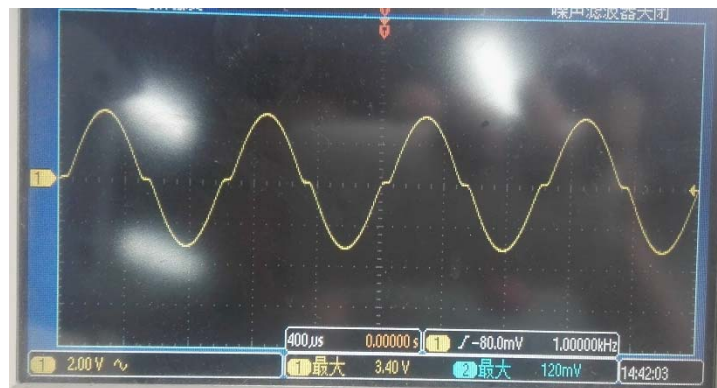
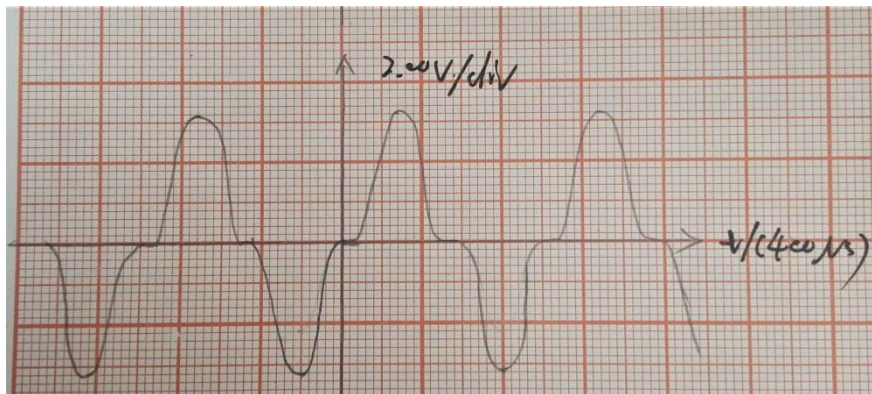


Figure 4 Waveform of cross over distortion

U_{CA} is less than 2.8V, so there must be cross over distortion.

Task 7

$U_i=4.5mV$ I measured output voltage and recorded as follow:

$R_L=0\Omega$ $R_C=470k\Omega$							
f(Hz)	50	100	300	400	500	600	700
20lgf(dB)	33.98	40.00	49.54	52.04	53.98	55.56	56.90
$U_{op}(mV)$	650	650	610	550	550	490	470
$U_o(mV)$	33.98	40.00	49.54	52.04	53.98	55.56	56.90
f(Hz)	730	800	900	1000	1500	2000	3000
20lgf(dB)	57.27	58.06	59.08	60.00	63.52	66.02	69.54

$U_{op}(mV)$	450	430	410	370	310	270	270
$U_o(mV)$	57.27	58.06	59.08	60.00	63.52	66.02	69.54
$R_L=470\Omega \quad R_c=0k\Omega$							
$f(Hz)$	80	150	250	350	450	800	1300
$20lgf(dB)$	38.06	43.52	47.96	50.88	53.06	58.06	62.28
$U'_{Op}(mV)$	90	110	110	130	130	150	130
$U'_O(mV)$	38.06	43.52	47.96	50.88	53.06	58.06	62.28
$f(Hz)$	2000	3000	3100	4000	5000	7000	10000
$20lgf(dB)$	66.02	69.54	69.83	72.04	73.98	76.90	80.00
$U'_{Op}(mV)$	230	390	330	370	410	410	450
$U'_O(mV)$	66.02	69.54	69.83	72.04	73.98	76.90	80.00

I plot the two amplitude frequency characteristic curves as figure 4:

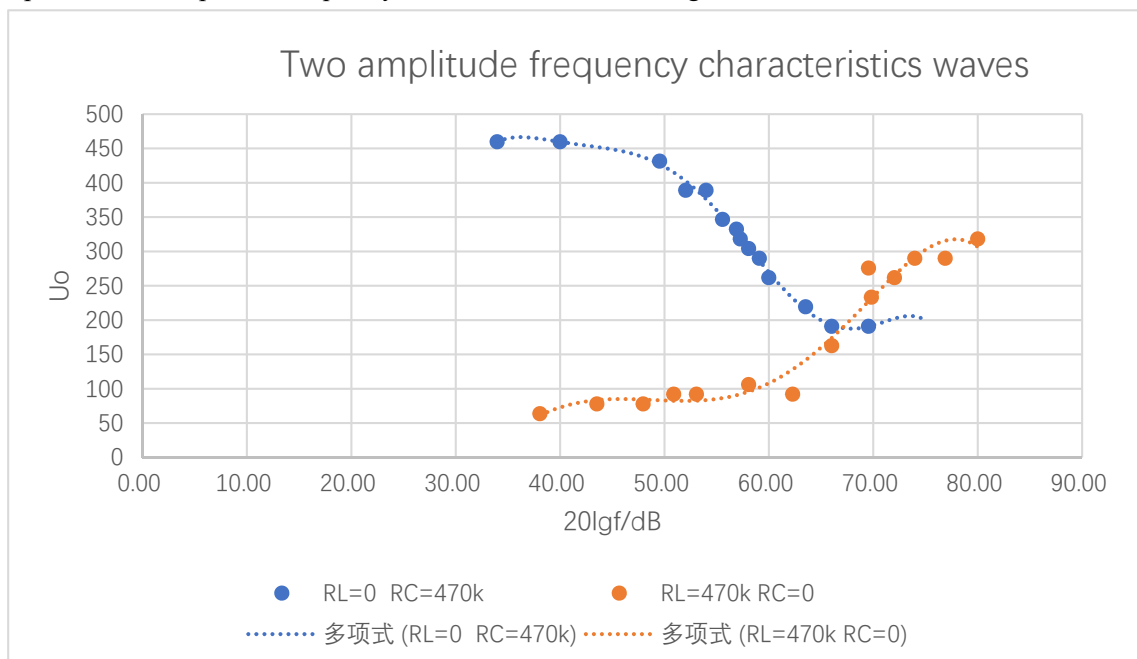


Figure 5 two amplitude frequency characteristic curves

Summary

I studied power amplifier through this experiment. The reason of cross over distortion is: when quiescent point is not suitable, input voltage plus quiescent voltage is too small to make triode work in enlargement area, so the initial part of sin wave becomes a straight line.